

Semi-conductor and Logic Gates

Lecture 21

Hyung-Sin Kim



SNU Graduate School of Data Science

Contents

- **Review**
 - **Bits, Data Types, and Operations**
- **Practice 14**
- **Semi-conductor**
- **Logic gates**
- **Combining logic gates**

Review

- **Bits, Data Types, and Operations**

Review

- Exact value vs. Presence/Absence
- Bit, multiple bits, and data types
- Logical variables, bit vectors, and operations
- Unsigned integers, signed integers, and operations
- Floating point, ASCII, and Hexagonal


Today's Goals

- We will explore computer hardware a little bit
- You will understand why semiconductor is the root of computers
- You will understand why computers only understands 0s and 1s
- You will understand how computer hardware perform logical operations, arithmetic operations, and store values
- You will understand that hardware can do everything software can do. It is just hard (fixed), instead of soft (flexible)

Semi-conductor

What is Semi-conductor

 - Something that is necessary for Korean economy
- Something that Samsung Electronics and SK Hynix are doing well
- Some rectangular stuff that is necessary for making computers



What is Semi-conductor


- Conductor: Any material that allows electric current to pass through it
 - Copper, Aluminum, Steel, etc...
- Insulator: Any material that does not allow electric current to pass through it
 - Plastic, Rubber, Glass, Wood, etc...
- **Semi-conductor:** A material that can act as a conductor or an insulator depending on conditions
- **Transistor:** A device built by using semi-conductor, which is a fundamental unit of computers




How does Transistor work?

- Left and right parts are connected or not depending on the gate status
 - n-type transistor

 If gate is supplied with **2.9 V**,
left and right are connected
like a conductor (wire)



 
If gate is supplied with **0 V**,
left and right are disconnected
like an insulator (disconnected wire)




How does Transistor work?

- Left and right parts are connected or not depending on the gate status
 - p-type transistor

 If gate is supplied with **0 V**,
left and right are connected
like a conductor (wire)



 If gate is supplied with **2.9 V**,
left and right are disconnected
like an insulator (disconnected wire)



*We can do **Boolean operation** with binary numbers
by arranging multiple transistors*

Logic gates


Logic Gates

NOT




INPUT		OUTPUT
A		
0		1
1		0

AND

 

INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

OR

 

INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

XOR




INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR

 

INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

XNOR




INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	1

NOT Gate (Inverter)

Input	Output
0	1
1	0


NOT

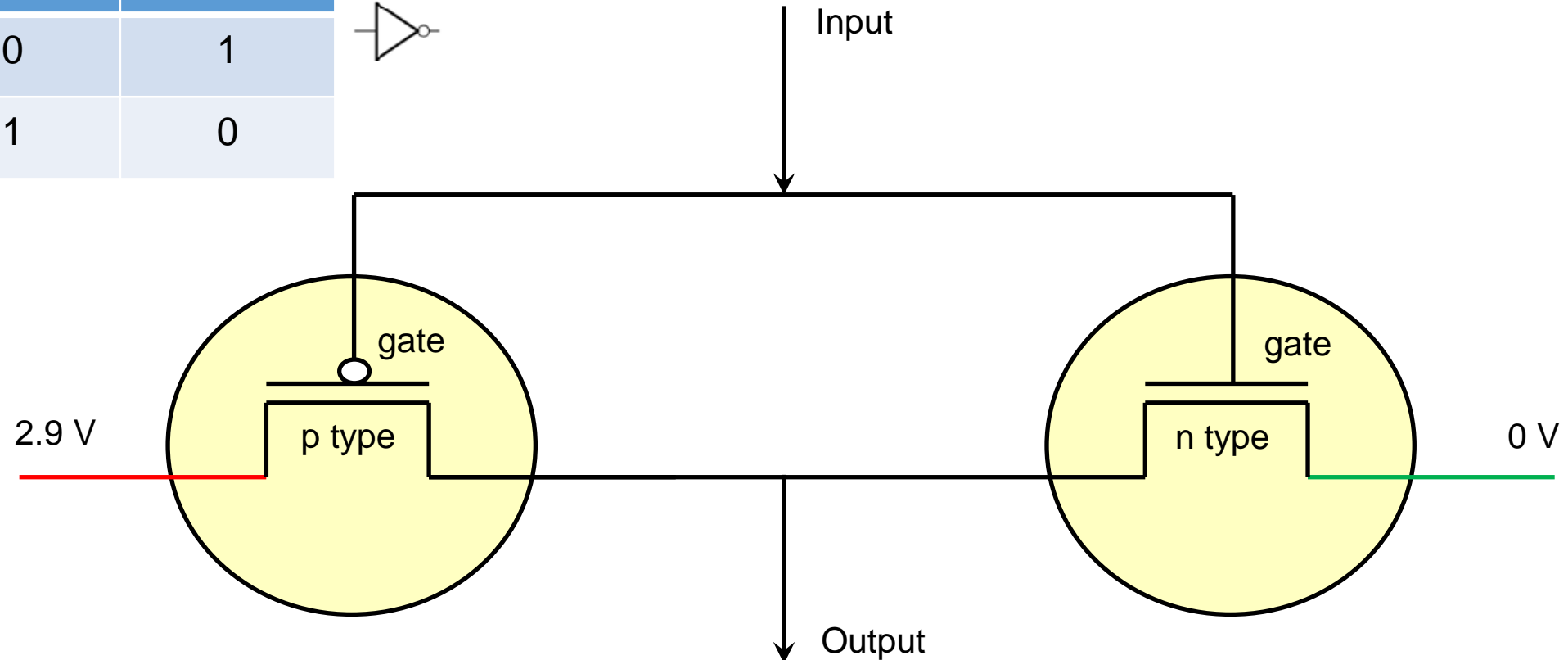

NOT Gate (Inverter) – For Input 0

Input	Output
0	1
1	0


NOT

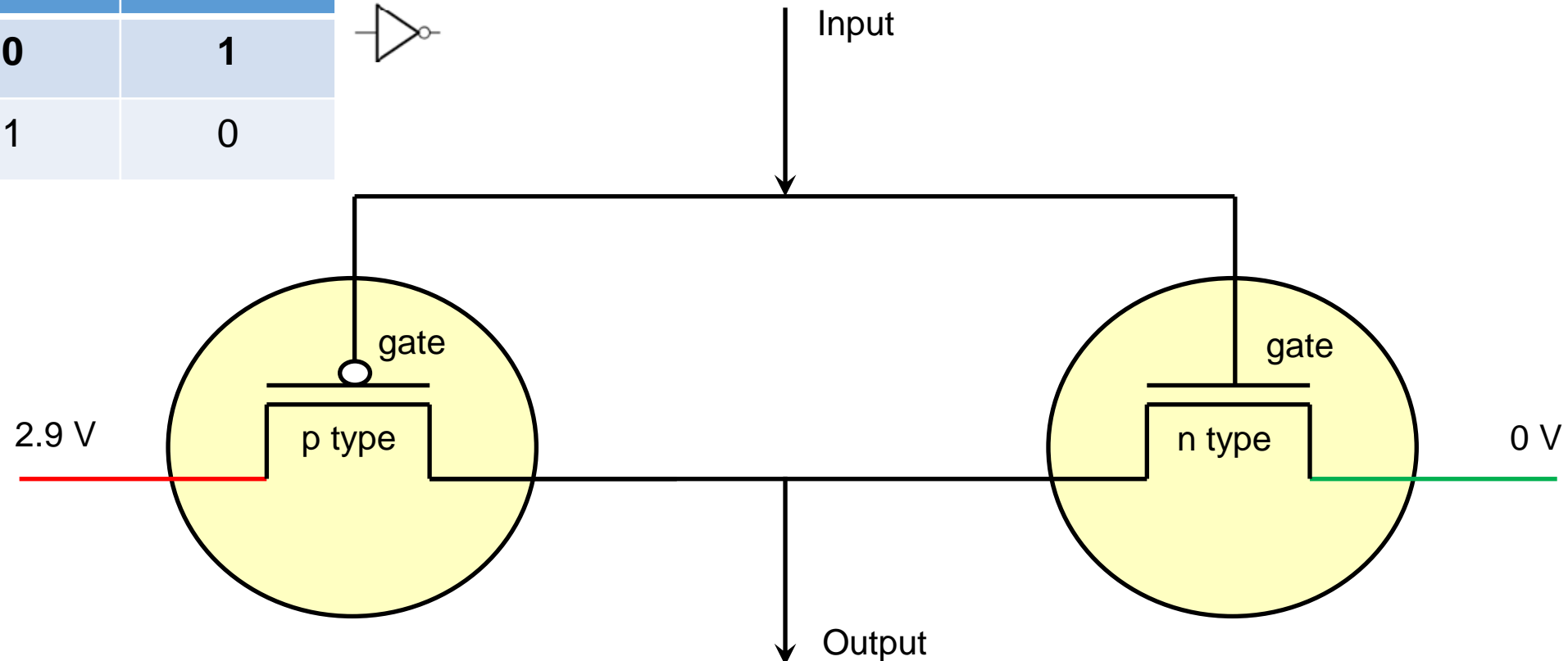

NOT Gate (Inverter) – For Input 0

Input	Output
0	1
1	0


NOT

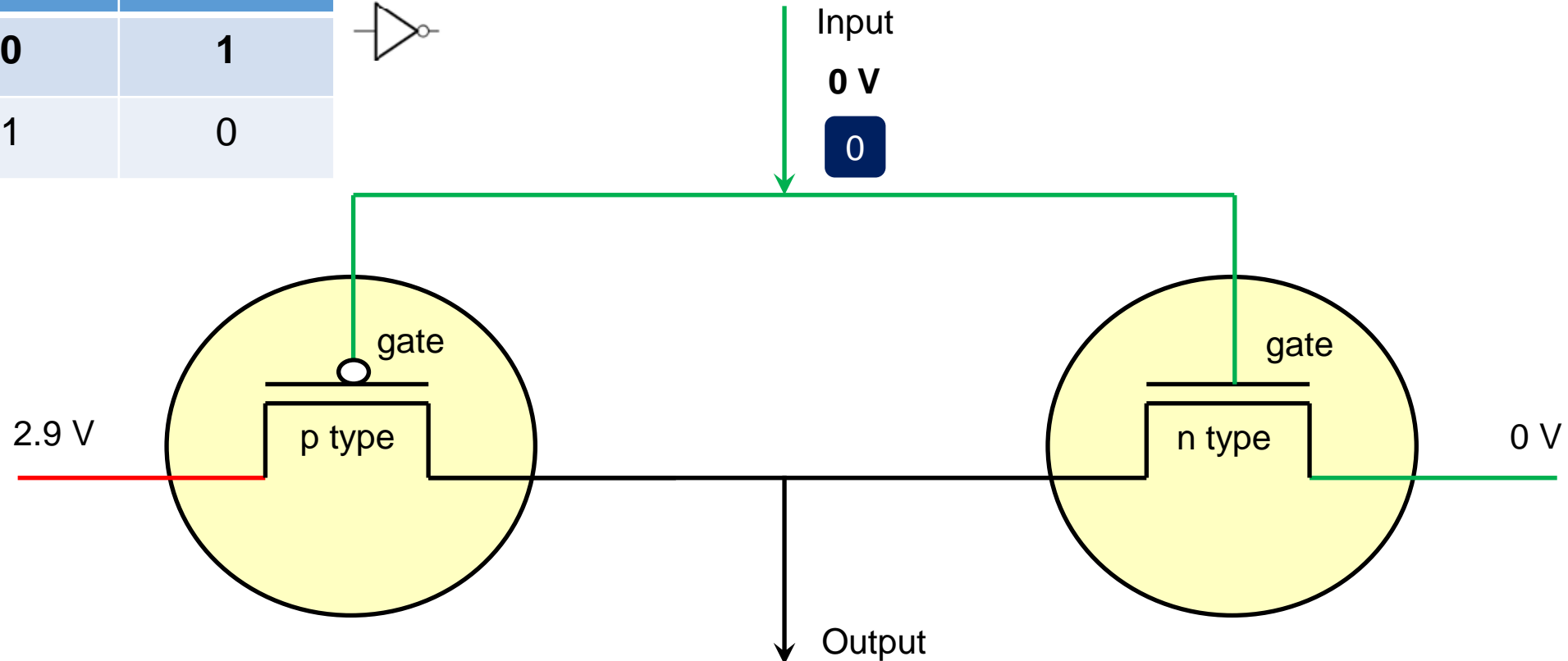

NOT Gate (Inverter) – For Input 0

Input	Output
0	1
1	0


NOT

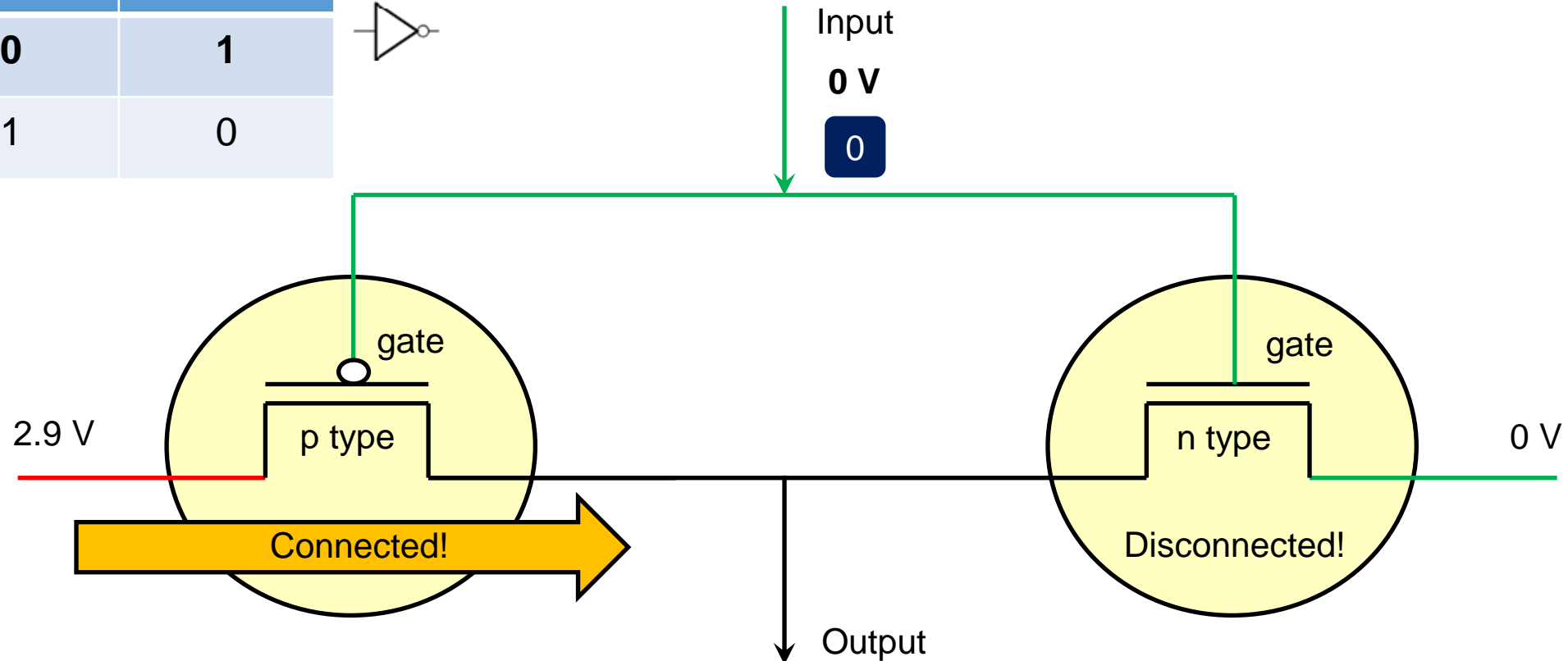

NOT Gate (Inverter) – For Input 0

Input	Output
0	1
1	0


NOT

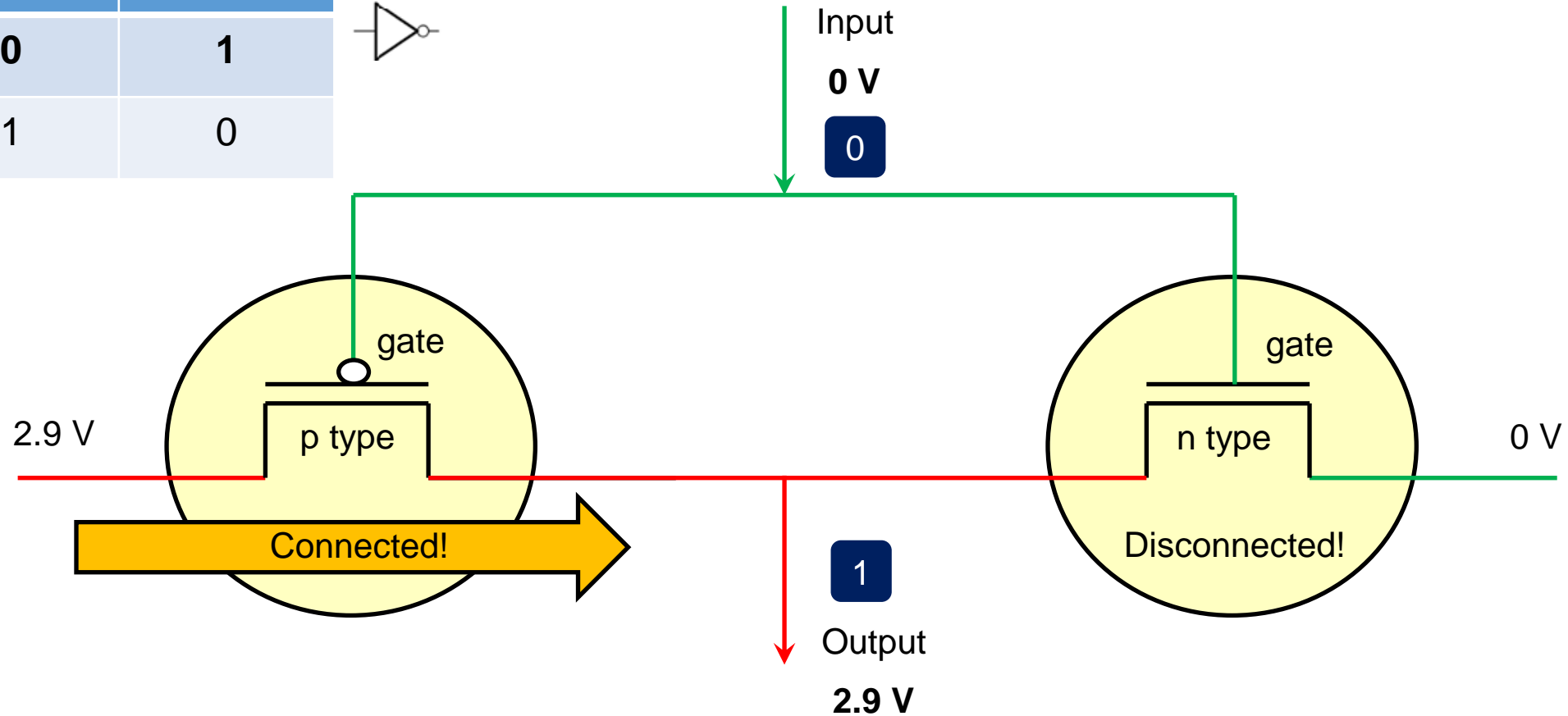

NOT Gate (Inverter) – For Input 1

Input	Output
0	1
1	0


NOT

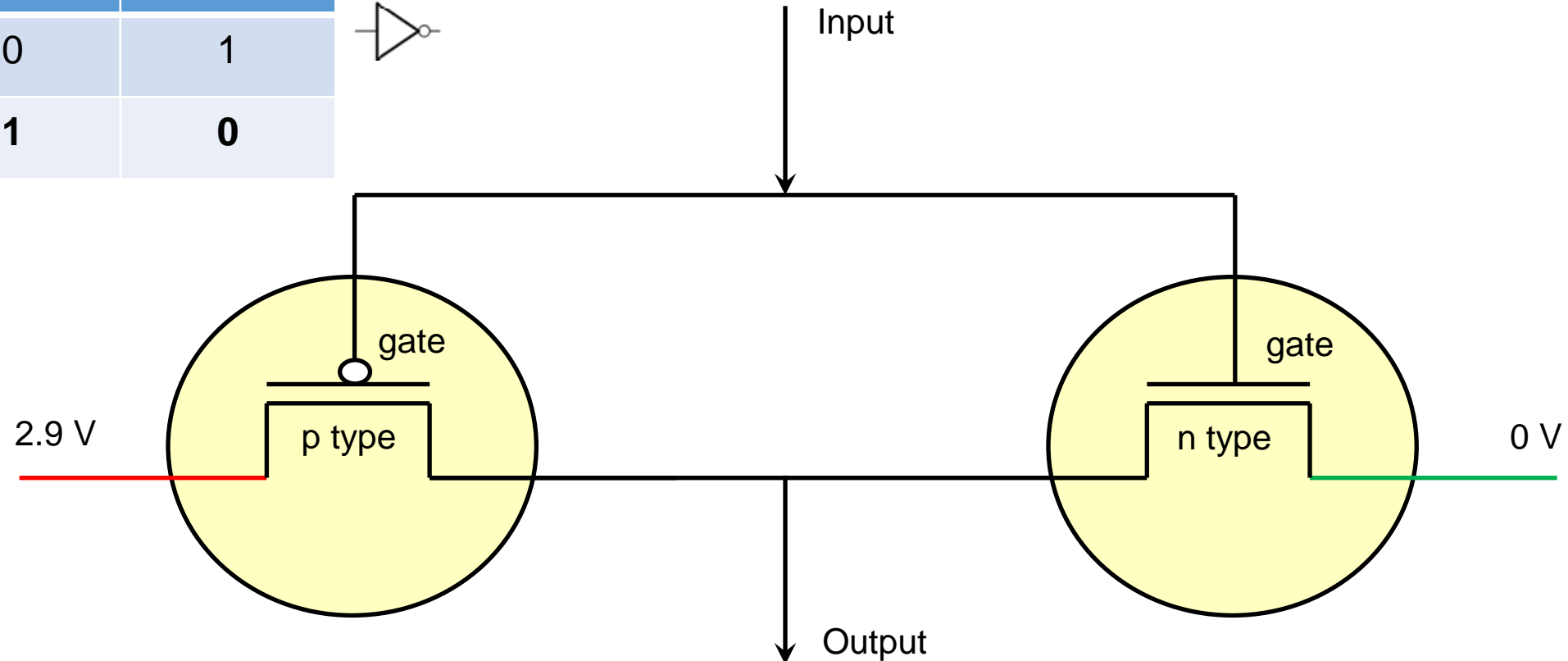

NOT Gate (Inverter) – For Input 1

Input	Output
0	1
1	0


NOT

 

NOT Gate (Inverter) – For Input 1

Input	Output
0	1
1	0


NOT

 


NOT Gate (Inverter) – For Input 1

Input	Output
0	1
1	0


NOT

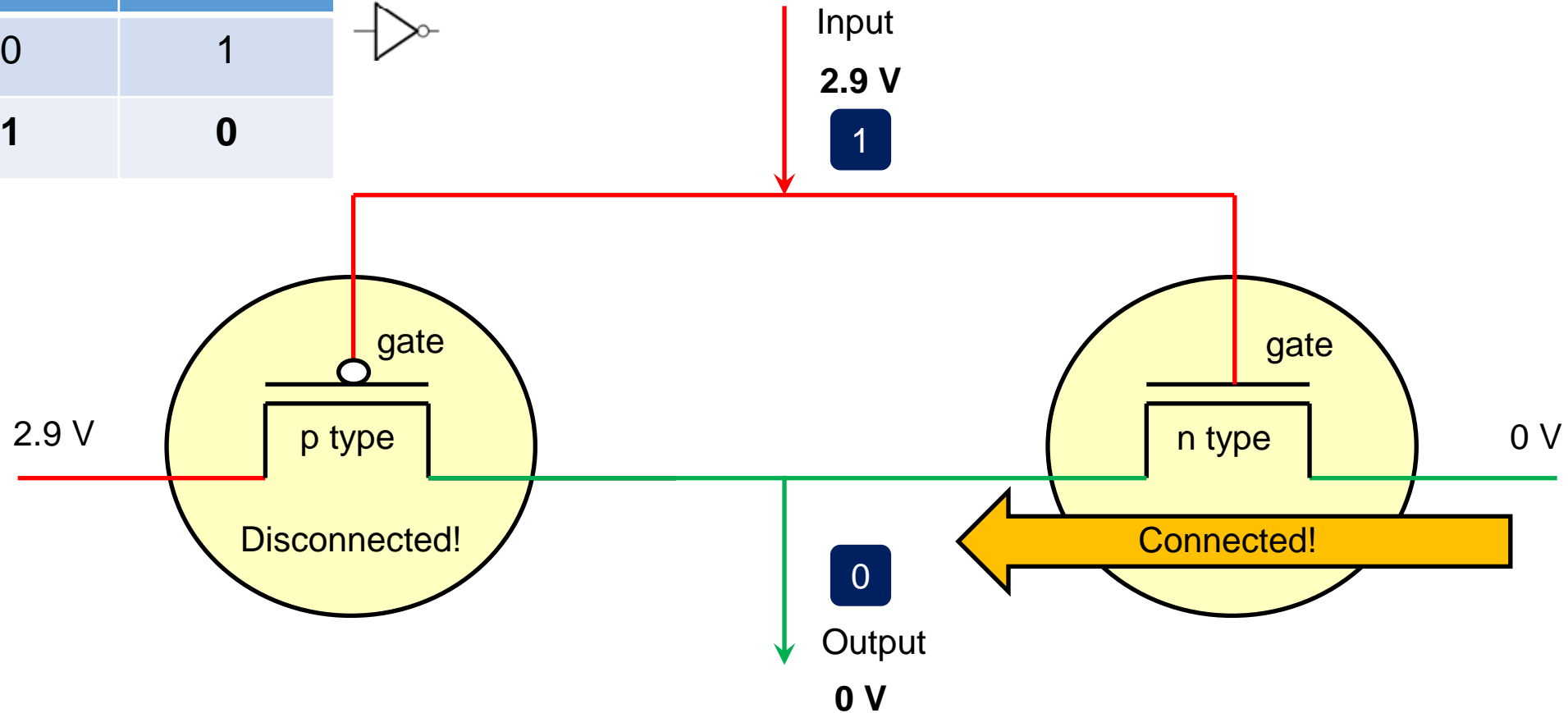


NOR Gate

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

 


NOR Gate – For Input (0, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

 


NOR Gate – For Input (0, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

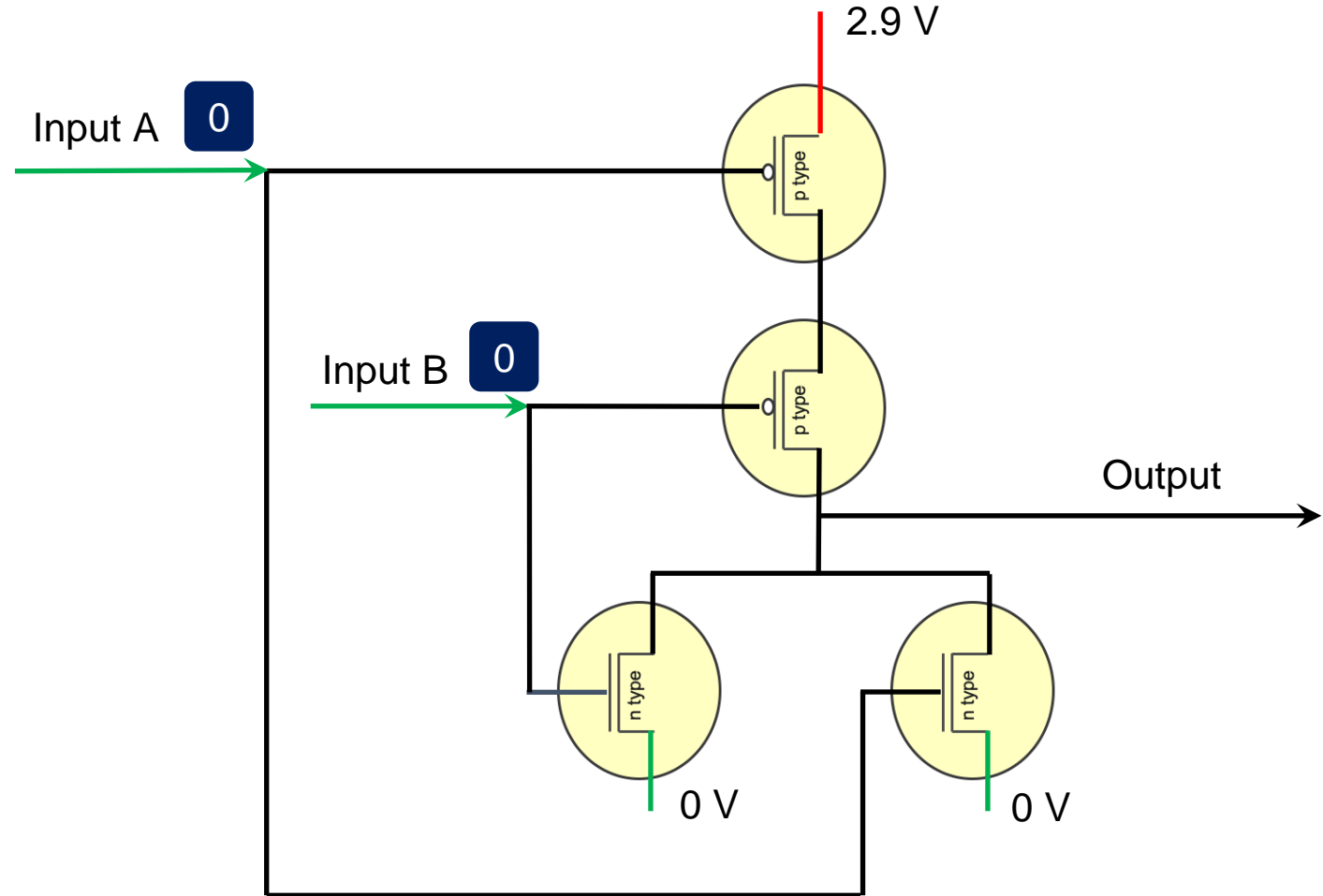


NOR Gate – For Input (0, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

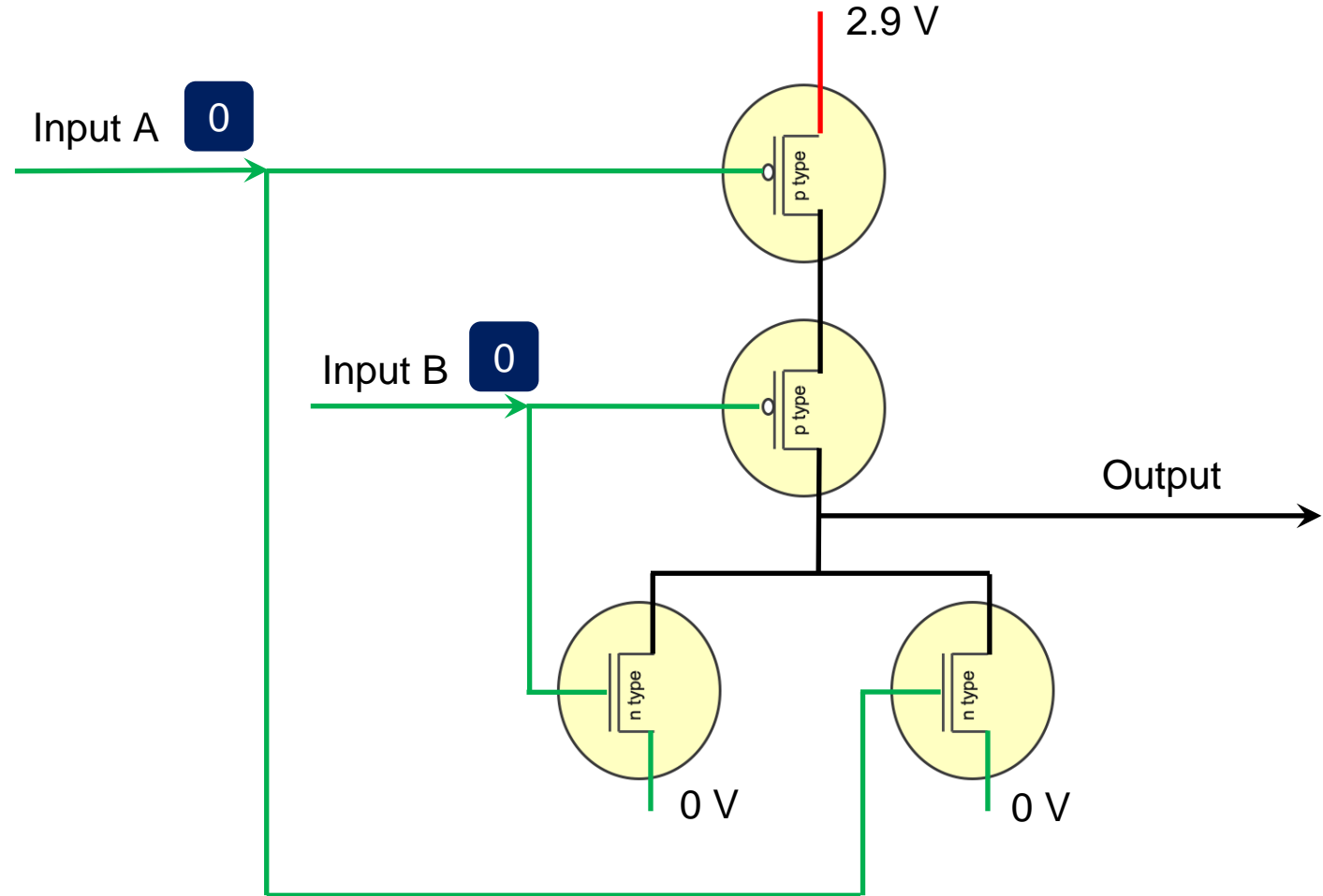


NOR Gate – For Input (0, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

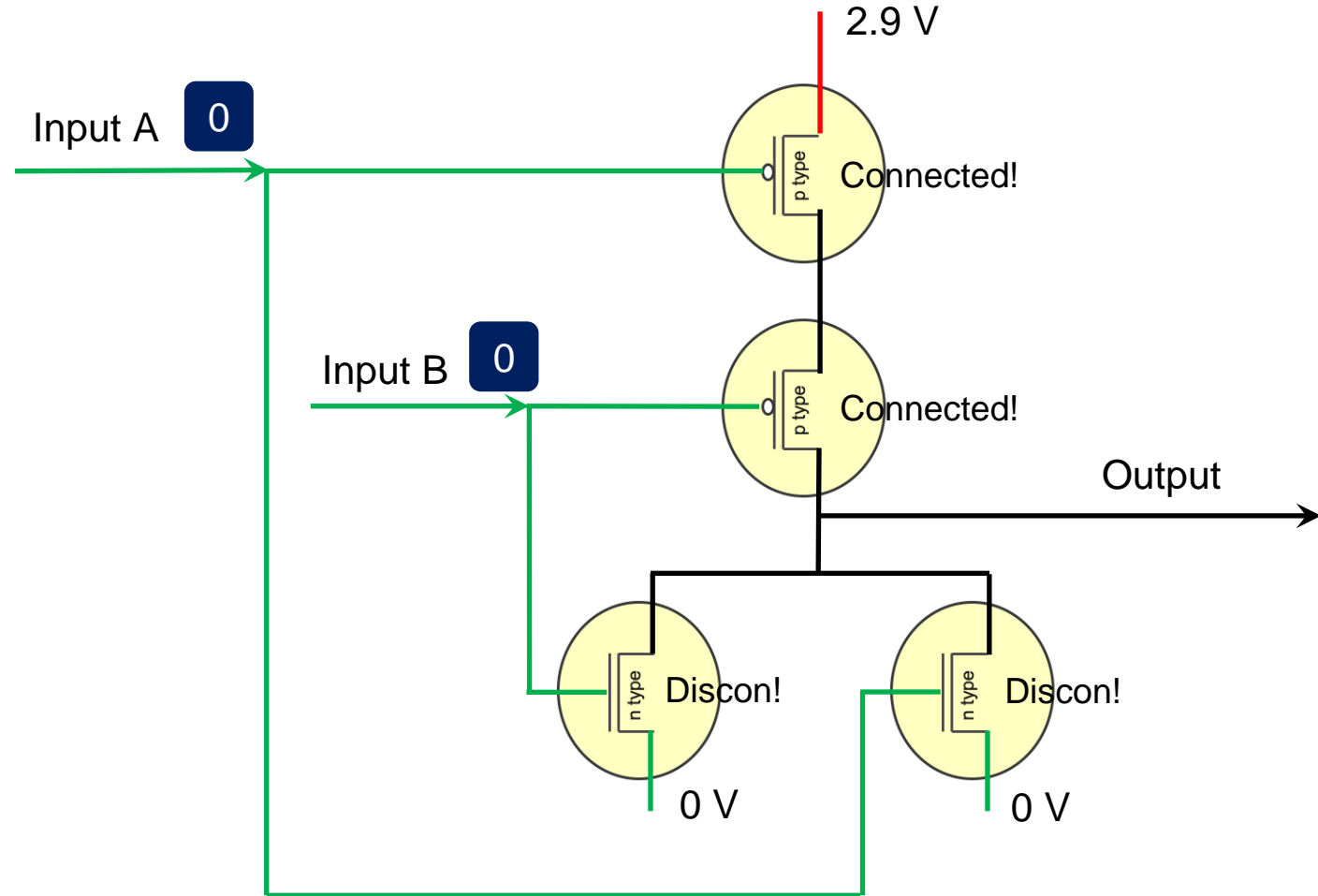


NOR Gate – For Input (0, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

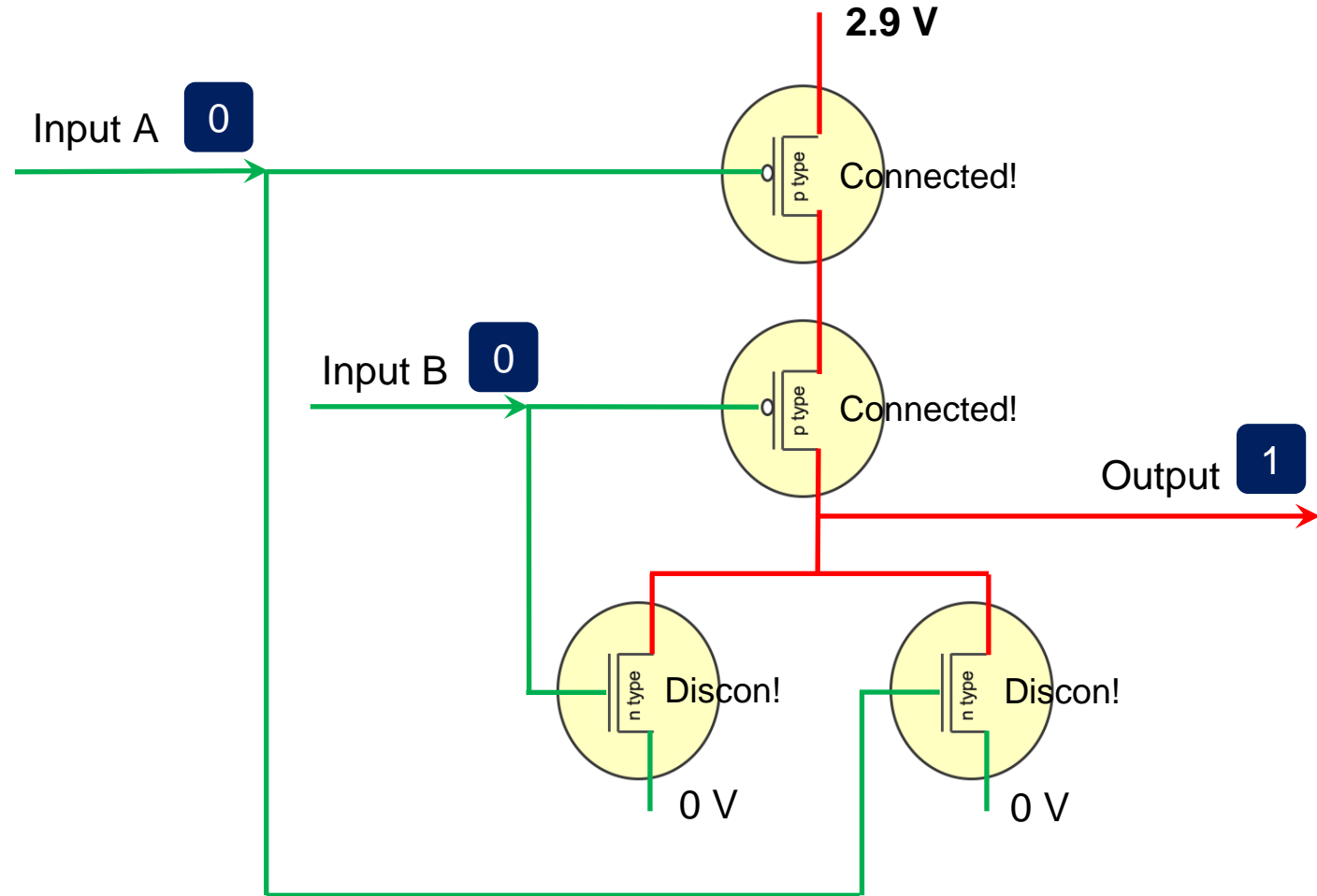


NOR Gate – For Input (1, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

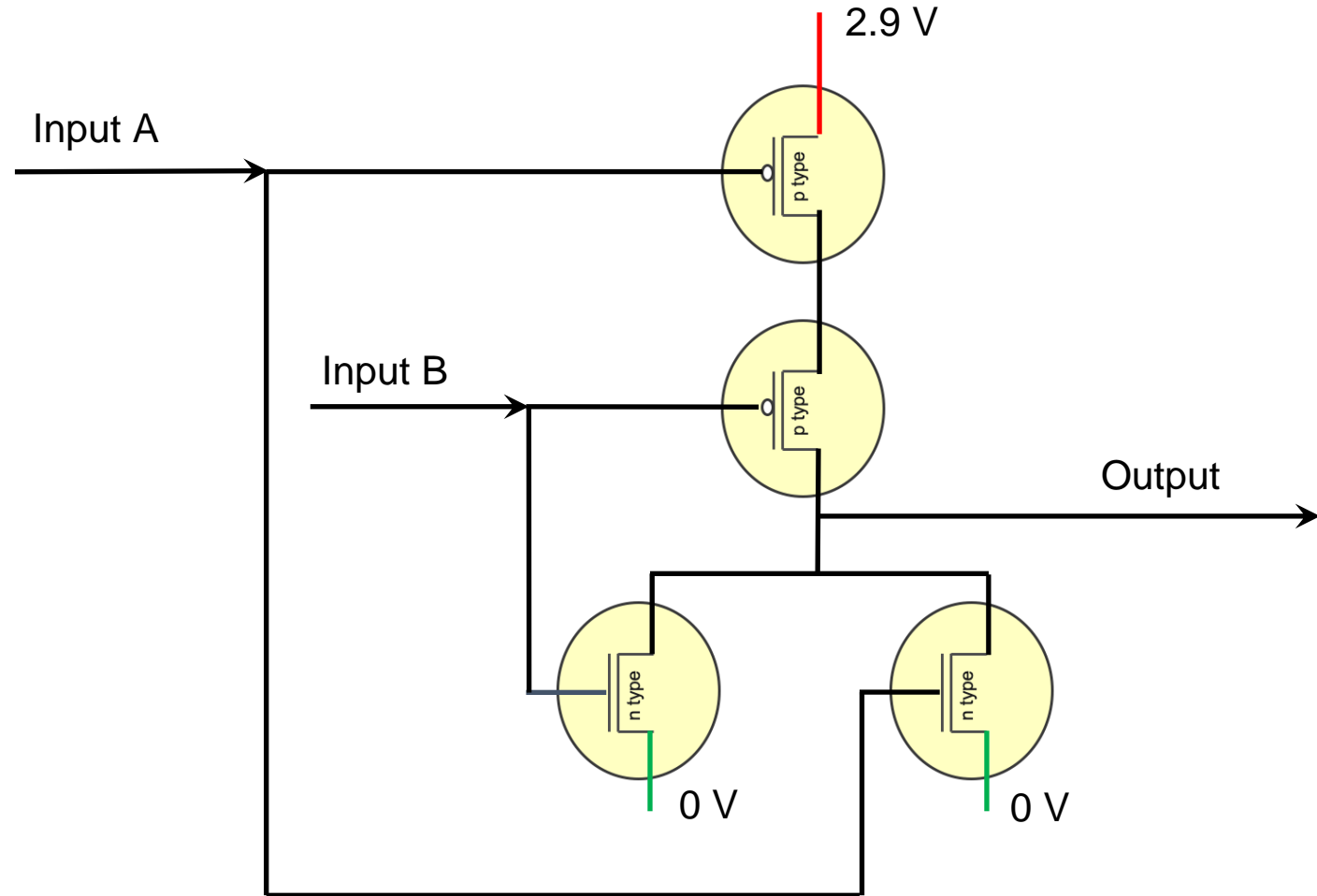


NOR Gate – For Input (1, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

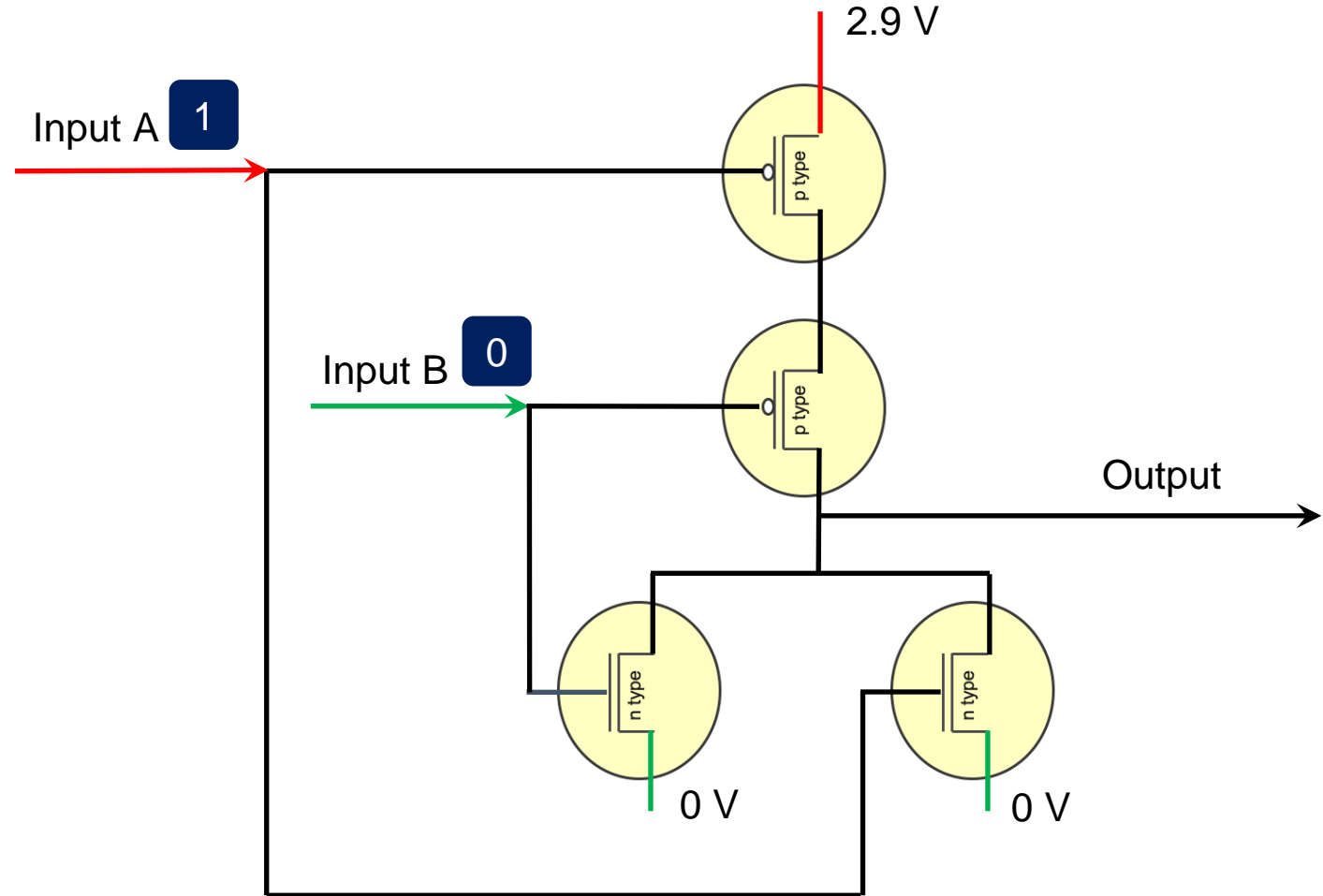


NOR Gate – For Input (1, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

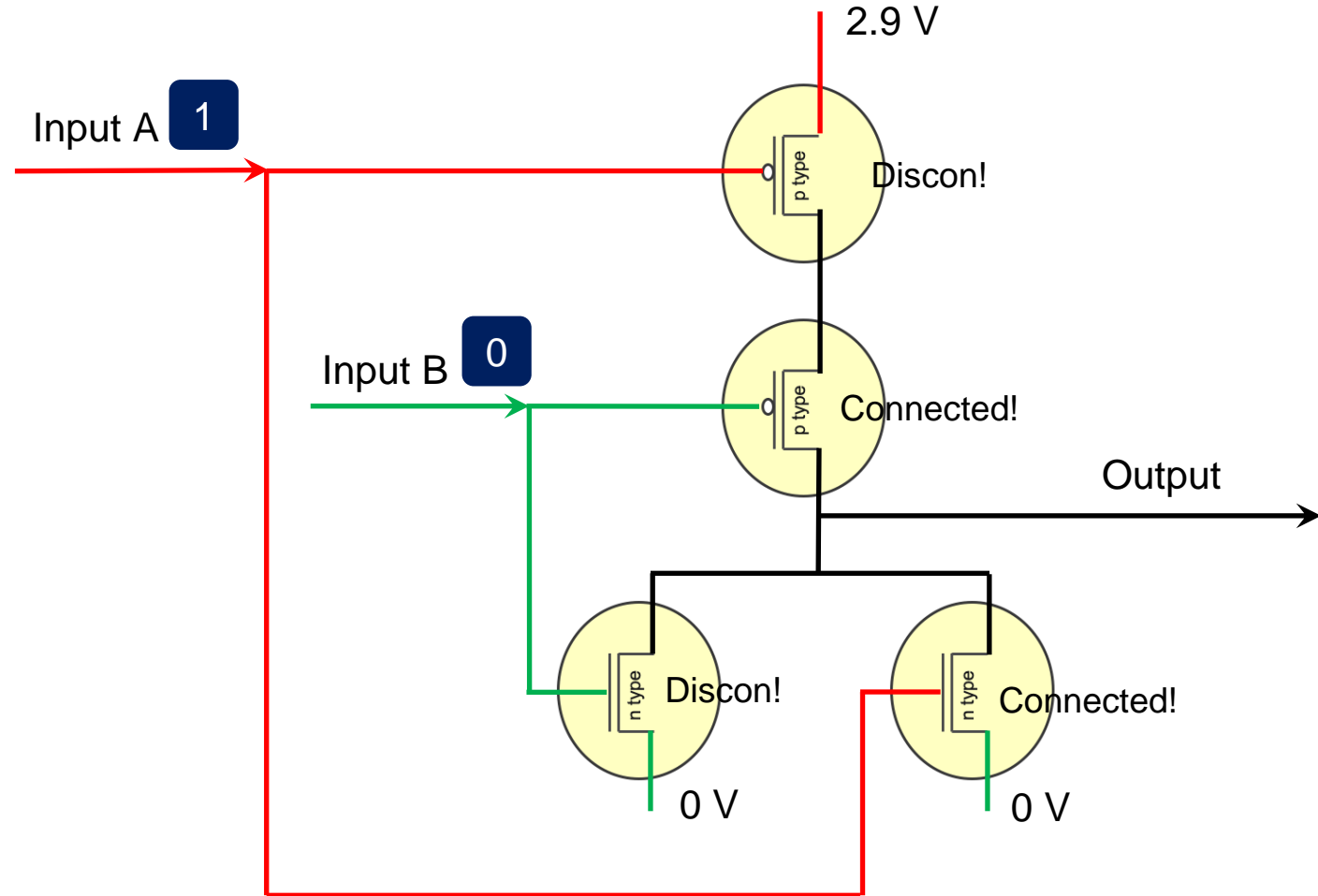


NOR Gate – For Input (1, 0)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

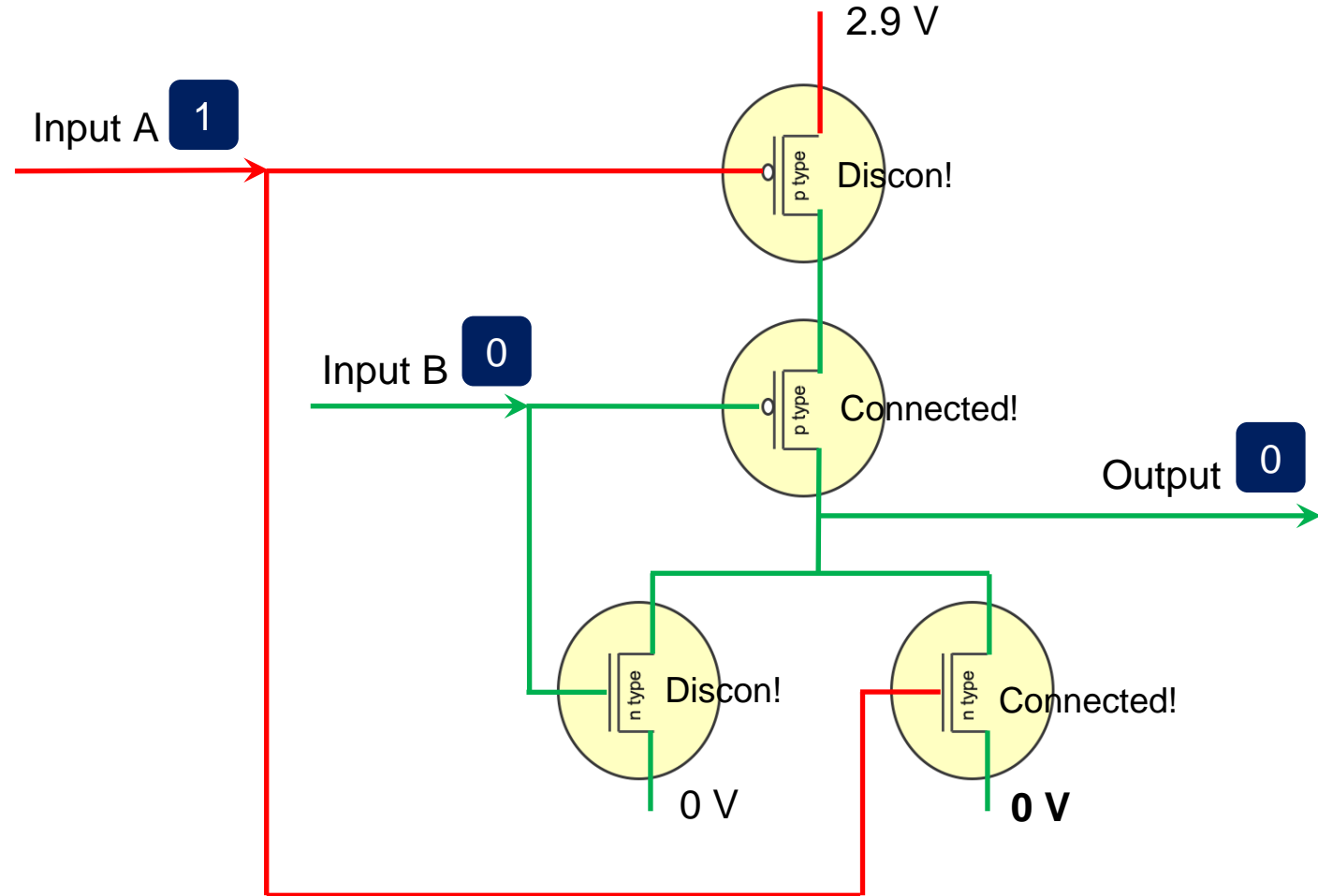


NOR Gate – For Input (0, 1)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

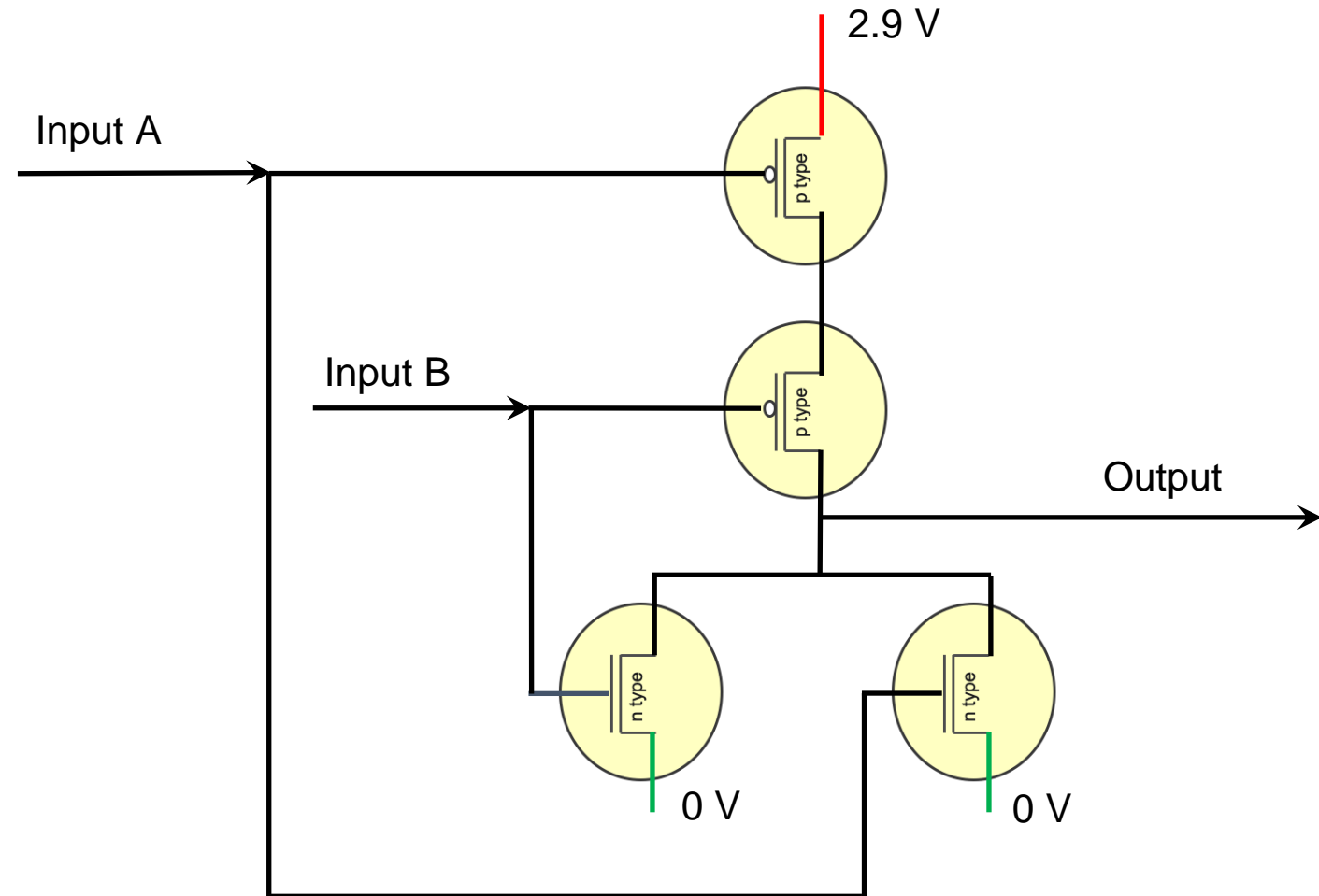


NOR Gate – For Input (0, 1)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

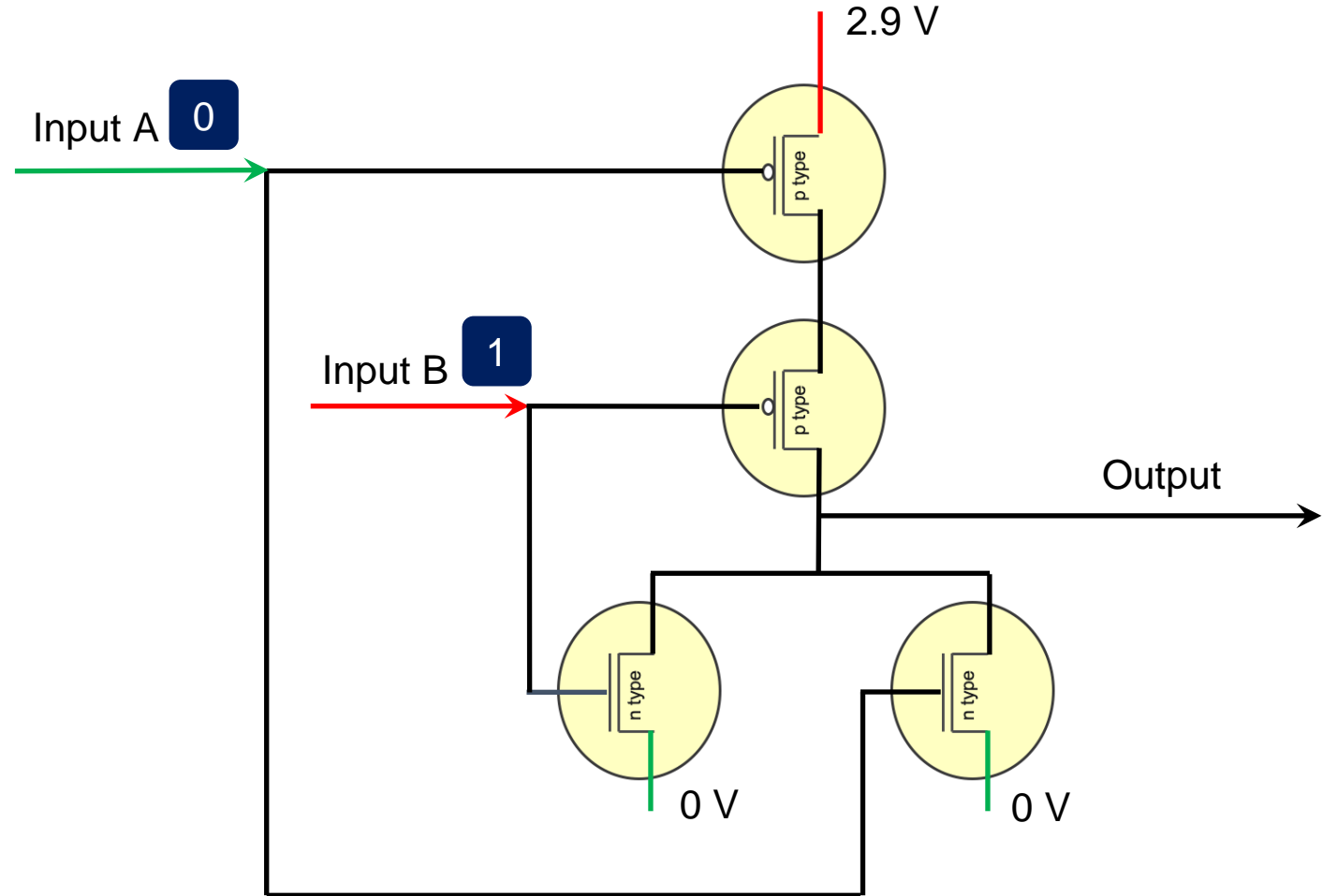


NOR Gate – For Input (0, 1)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

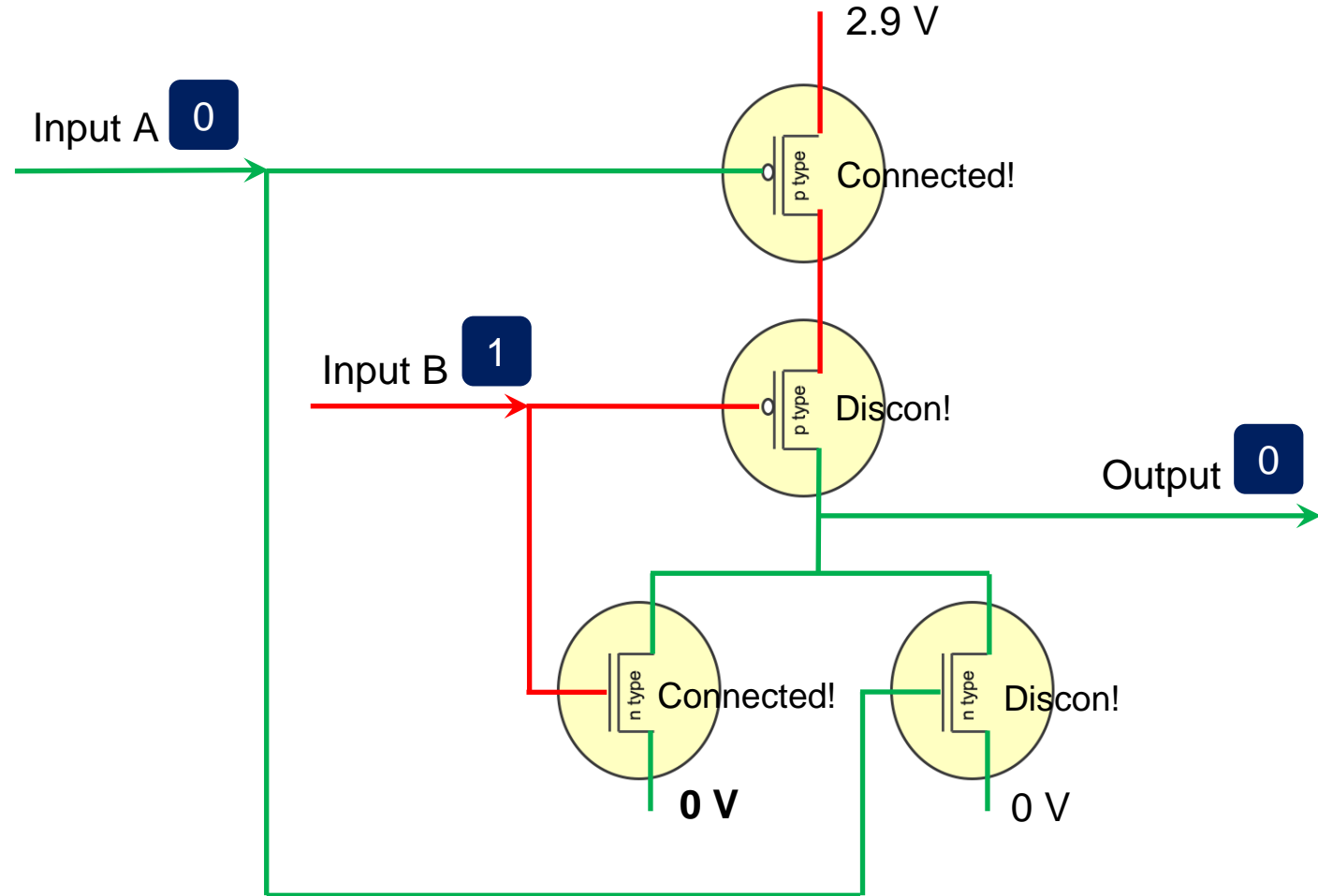


NOR Gate – For Input (1, 1)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

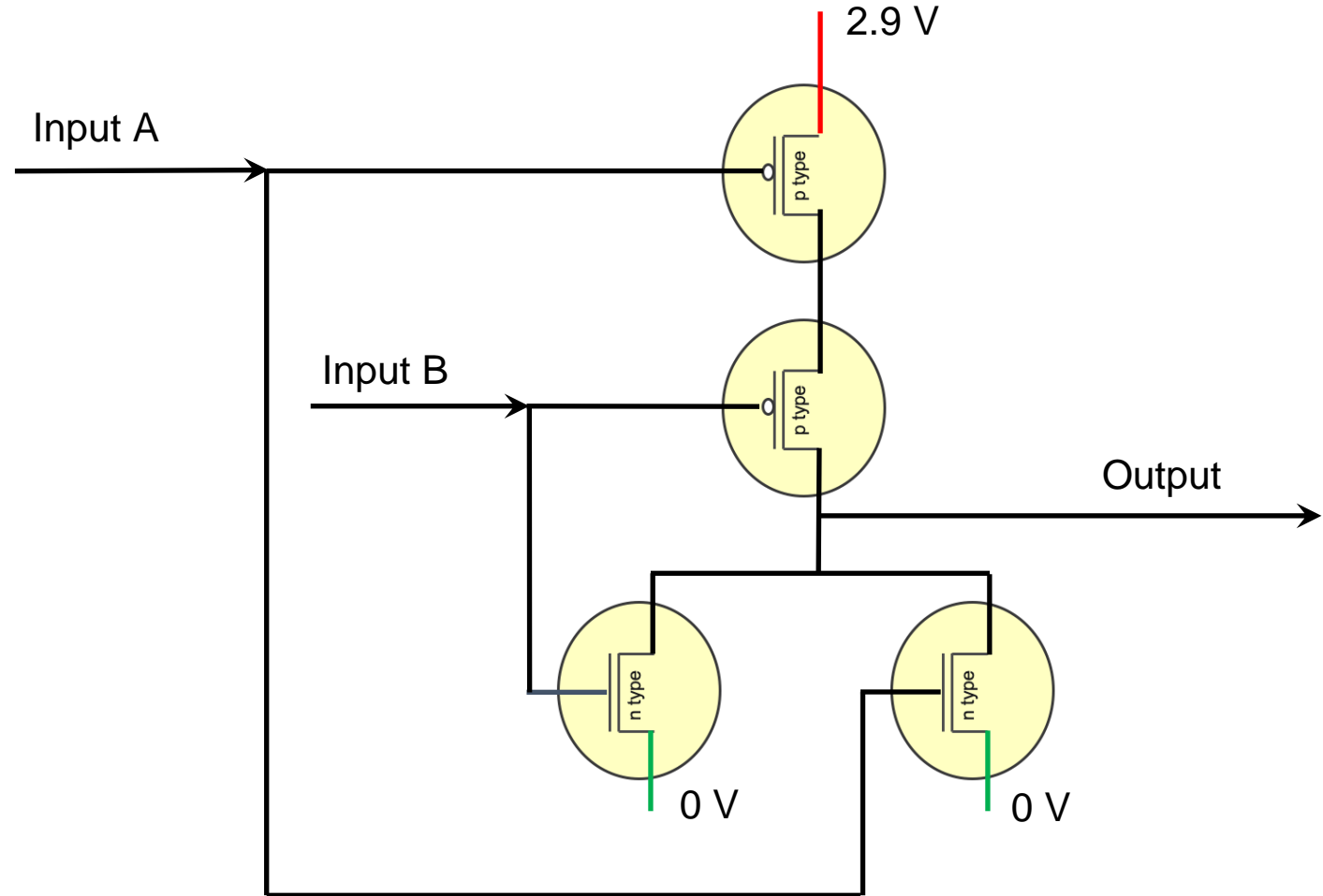


NOR Gate – For Input (1, 1)

 


Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

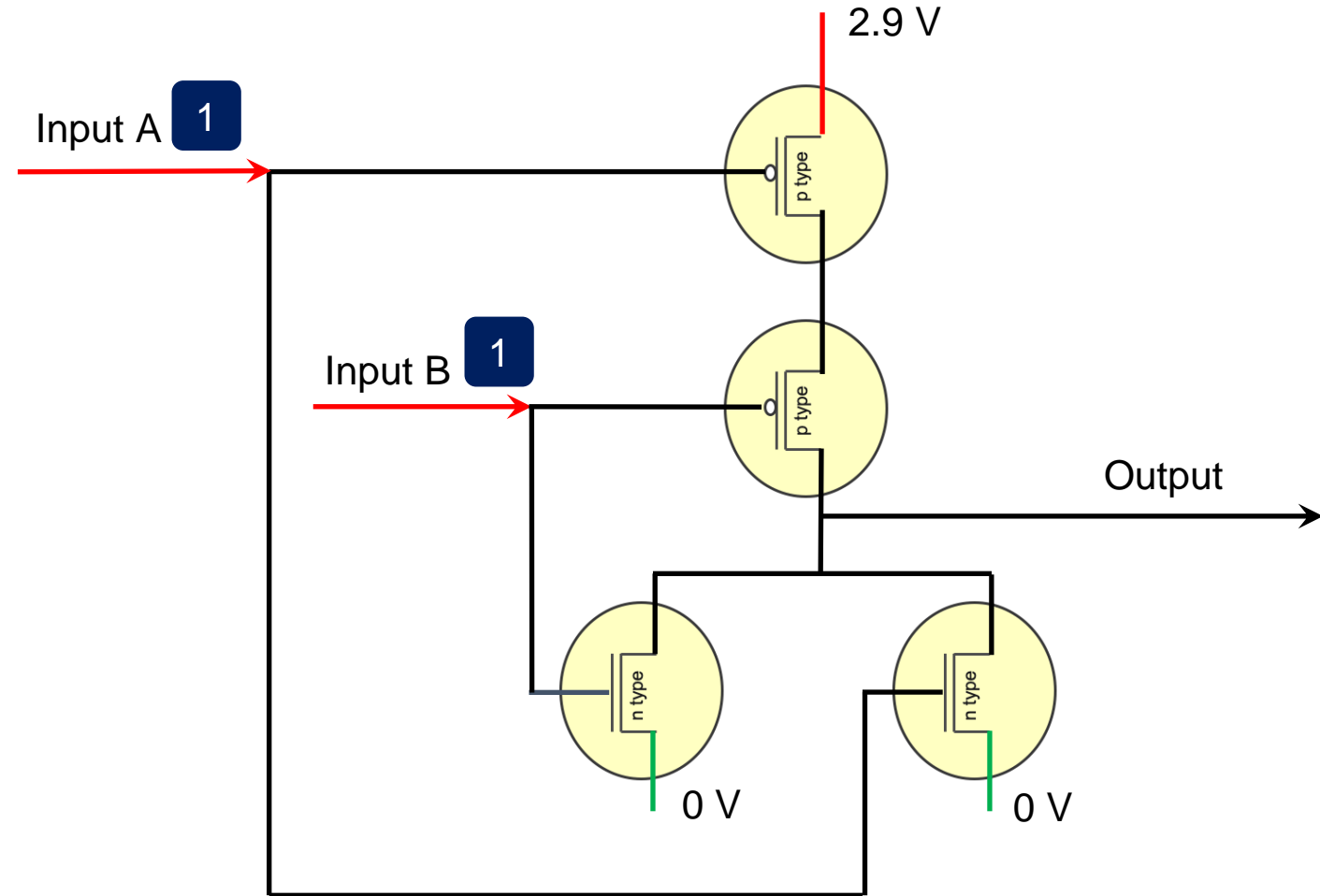

NOR Gate – For Input (1, 1)

 

Input A	Input B	Output
0	0	1
1	0	0
0	1	0
1	1	0

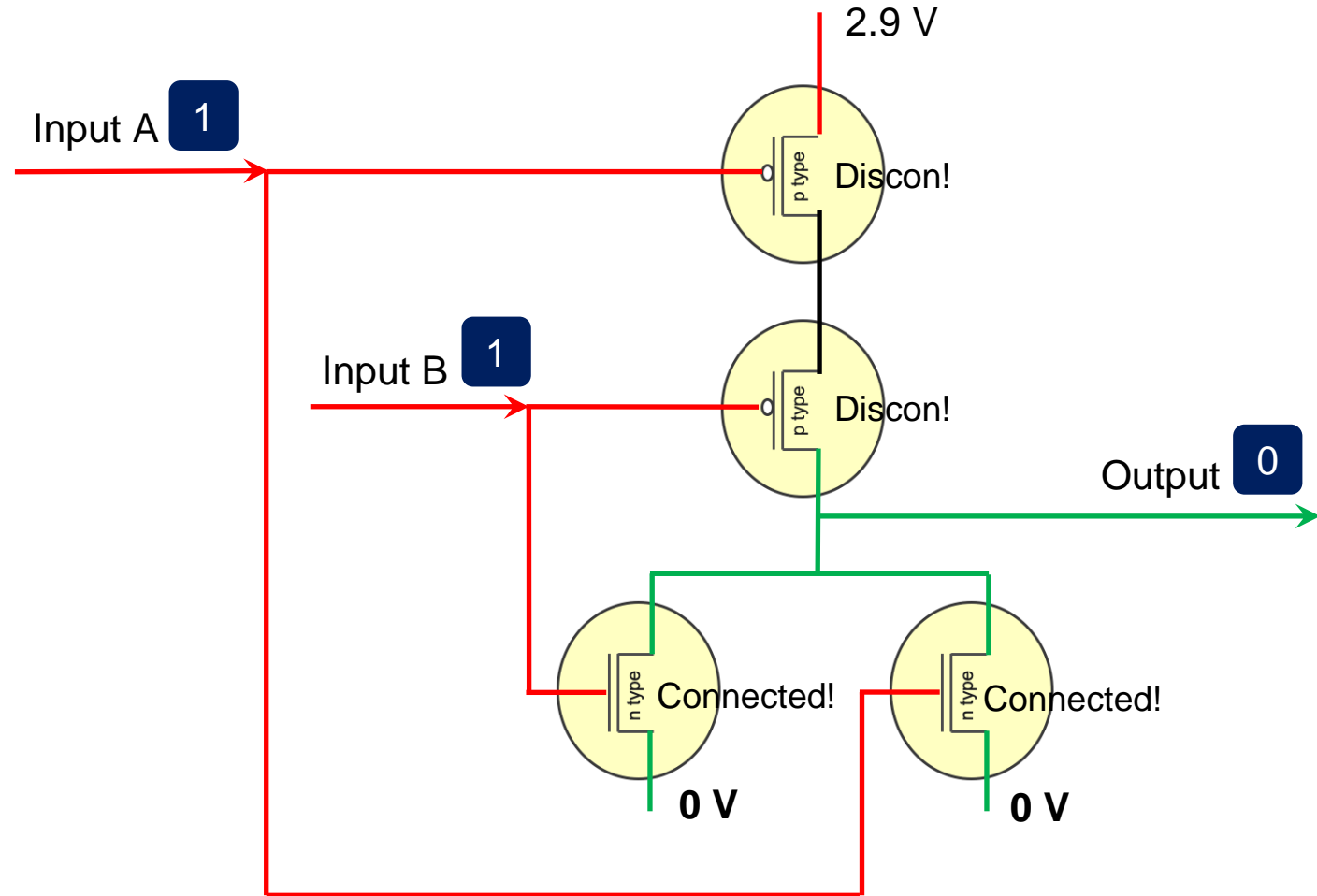


Combining logic gates

*By combining the basic logic gates,
We can do more general **binary computation!***

1-bit Binary (Half) Adder

- Adding two unit binary digits (no carry as an input)


A	B	Sum	Carry
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

 

1-bit Binary (Full) Adder

- Adding two i -th binary digits (with carry input)



A_i	B_i	$Carry_i$	Sum_i	$Carry_{i+1}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

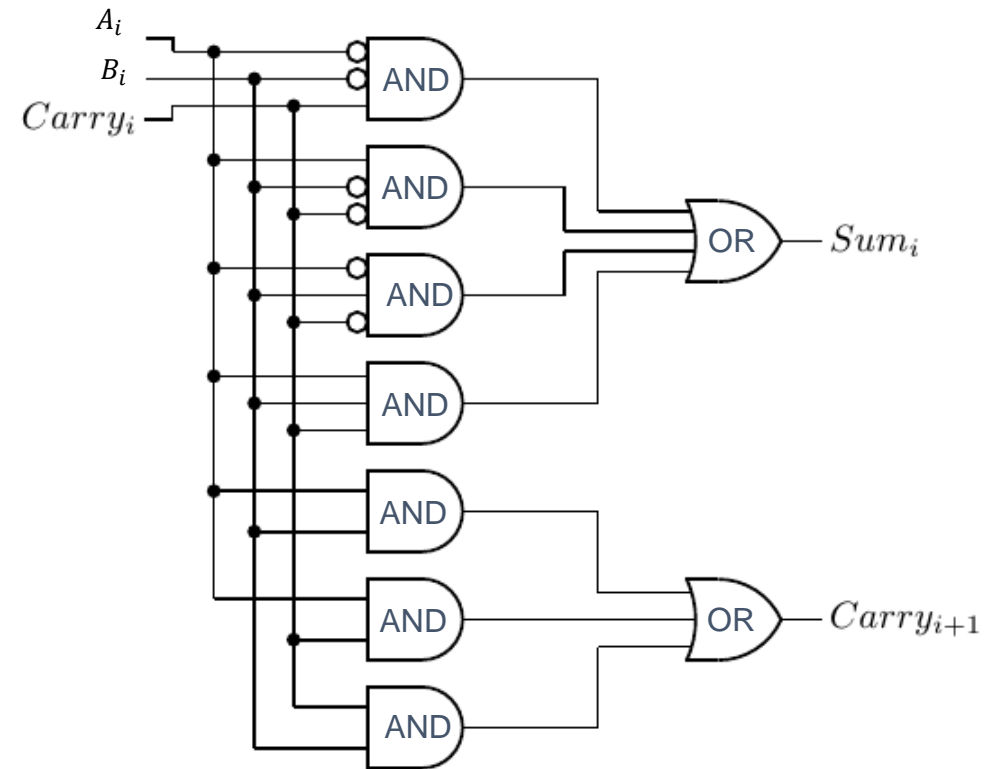

*We can even **store** binary information by arranging multiple transistors (i.e., memory)*

R-S Latch – Overview

  
- Q is the binary value that R-S Latch stores
 - Q' is the complement of Q
- Set and Reset are 0 most of the time
 - Each can be 1 for a short time (pulse)



- When Set=1, 1 starts to be stored in Q
- When Reset=1, 0 starts to be stored in Q



R-S Latch – Steady State

- $Q = 0$ is stored

 



R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0
 - Upper NOR gate makes Q become 1





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0
 - Upper NOR gate makes Q become 1





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0
 - Upper NOR gate makes Q become 1
 - Set goes back to 0





R-S Latch – Store binary value 1

  - Input a binary pulse to “Set”
 - Set becomes 1
 - Lower NOR gate makes Q' become 0
 - Upper NOR gate makes Q become 1
 - Set goes back to 0
 - Now the latch goes back to the steady state
 - But stores binary value 1





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0
 - Lower NOR gate makes Q' become 1





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0
 - Lower NOR gate makes Q' become 1





R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0
 - Lower NOR gate makes Q' become 1
 - Reset goes back to 0



R-S Latch – Store binary value 0

  - Input a binary pulse to “Reset”
 - Reset becomes 1
 - Upper NOR gate makes Q become 0
 - Lower NOR gate makes Q' become 1
 - Reset goes back to 0
 - Now the latch goes back to the steady state
 - But stores binary value 0




Memory

- Memory has a number of uniquely identifiable memory locations
 - Each location has its own **address**
 - Each location stores a fixed number of bits, **one byte** (called **addressability**)
- A location's address is represented as a bit sequence
- You can write (or read) an information to (or from) the memory location by using the location's address (circuits for the other locations are closed!)

Memory


- Memory has a number of uniquely identifiable memory locations
 - Each location has its own **address**
 - Each location stores a fixed number of bits, **one byte** (called **addressability**)
- A location's address is represented as a bit sequence
- You can write (or read) an information to (or from) the memory location by using the location's address (circuits for the other locations are closed!)

942-416 (01010101...)

 


Memory

- Memory has a number of uniquely identifiable memory locations
 - Each location has its own **address**
 - Each location stores a fixed number of bits, **one byte** (called **addressability**)
- A location's address is represented as a bit sequence
- You can write (or read) an information to (or from) the memory location by using the location's address (circuits for the other locations are closed!)

 

For More Details...

 - Textbook - Chapter 3
- Logic gate courses provided by ECE and CS
 - You will have a chance to play with FPGA



Summary

Summary

- Thanks to semi-conductor, we can convert a continuous voltage value to a binary value (analog to digital conversion)
- By combining transistors, we can build hardware that can **compute** and **store** binary values
- Today's CPU has about 3 billion transistors to perform complex tasks fast !

Software vs. Hardware


- If we can build software that can do a task, we can also build hardware that can do the same task
- Once you build the hardware for a task,
 - The hardware will do the task **super fast**
 - But it can do only the specific task... to do another task, you need to build another “computer”
- Once you build software for a task,
 - The software will do the task relatively slower than hardware
 - But you can **easily build another** software (i.e., programming) without building another computer

Software Hardware


- There are various tasks that people want to do by using computers
- It is important to **synergistically** use hardware and software to do these tasks
- If a task is well defined and needs to be done very frequently and fast, we can make it “**hard**”
 - It would be good to build a hardware component specialized for the specific task
- If not, we need flexibility to do the task, treating it “**soft**”ly

CPU ❤️ Accelerators

 - CPU is a processing unit that can execute general software instructions
 - Wide applications but slow performance



 - Accelerator is a processing unit that is optimized for specific types of operations
 - Limited applications but fast performance (GPU, mobile GPU, TPU, edge TPU...)



Q&A

Any questions?

Thanks!